

ACHARYA MOTIBHAI PATEL INSTITUTE OF COMPUTER STUDIES

Practical Examination

SET-A

Programme	DD(BCA-MCA)		
Subject	U51C4IDE - Introduction to Digital Electronics	Semester	I
Duration	1 Hour	Total Marks	10

Instructions: Attempt all questions. Each question carries 5 marks. Write SQL queries with correct and complete syntax.

Q.1 Implement all **Basic Gates**.

OR

Prove **De Morgan's First and Second Theorem**.

Q.2 Implement **2 × 1 Multiplexer**.

— End of Question Paper —

SET-B

Programme	DD(BCA-MCA)		
Subject	U51C4IDE - Introduction to Digital Electronics	Semester	I
Duration	1 Hour	Total Marks	10

Instructions: Attempt all questions. Each question carries 5 marks. Write SQL queries with correct and complete syntax.

Q.1 Implement all **Universal Gates**.

OR

Prove **De Morgan's First and Second Theorem**.

Q.2 Implement **2 × 1 Multiplexer**.

— End of Question Paper —